

EXPERIMENT 3 Resistors in Series and in Parallel

Data Page Student _____

Instructions: Print 2 copies of this page to use in class

$R_1 = \underline{\hspace{2cm}} \pm \underline{\hspace{1cm}}$, $R_2 = \underline{\hspace{2cm}} \pm \underline{\hspace{1cm}}$, $R_3 =$
 $\underline{\hspace{2cm}} \pm \underline{\hspace{1cm}}$

Circuit	measured R (ohm)	calculated R (ohm)	difference (ohm)	percent error
Figure 2				
Figure 3				
Figure 4				
Figure 5				