

Physics 281    **EXPERIMENT 3**  
**Resistors in Series and in Parallel**

---

**STUDENT** \_\_\_\_\_

**DATE** \_\_\_\_\_

**PARTNER(s)** \_\_\_\_\_

\_\_\_\_\_

---

**The goals of experiment**

---

**Theoretical background**

---

**Sketch of experimental set-up**

---

**PROCEDURE (use more paper if needed)**